

INEL 3105 lecture #19.

Note Title

11/10/2009

$$\textcircled{3} \text{ Condensadores: } i_c(t) = C \frac{dV_c(t)}{dt}$$

$$i_c(t) = I_m e^{j(\omega t + \theta_i)}$$

$$V_c(t) = V_m e^{j(\omega t + \theta_v)}$$

$$I_m e^{j\theta_i} = C \frac{d}{dt} [V_m e^{j\omega t} e^{j\theta_v}] = C V_m e^{j\theta_v} j\omega e^{j\omega t}$$

$$I_m e^{j\theta_i} = j\omega C V_m e^{j\theta_v}$$

fasor de i_c
fasor de V_c


$$\hat{I}_c = j\omega C \hat{V}_c \Rightarrow \boxed{Z_c = \frac{1}{j\omega C}} \quad \text{IMPEDANCIA CAPACITIVA.}$$

$$\hat{V}_c = Z_c \hat{I}_c$$

$$I_m e^{j\theta_i} = j\omega C V_m e^{j\theta_v}$$

$$= \omega C V_m [1 e^{j\pi/2}] e^{j\theta_v} = \underbrace{\omega C V_m}_{I_m = \omega C V_m} e^{j(\theta_v + \pi/2)}$$



$\theta_i = \theta_v + \pi/2$

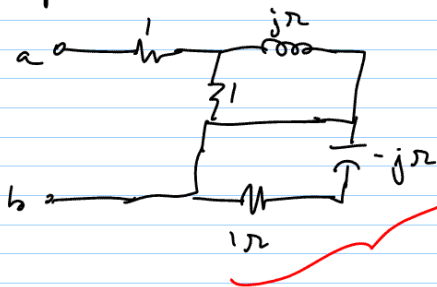Ejemplo: Evaluar Z_{ab} 


$$Z_L = j\omega L ; \omega L = 1$$

$$Z_C = -j \left(\frac{1}{\omega C} \right) ; (\omega C)^{-1} = 1$$


$$Z_1 = 1 - j$$

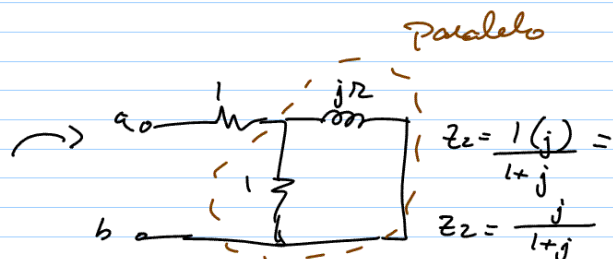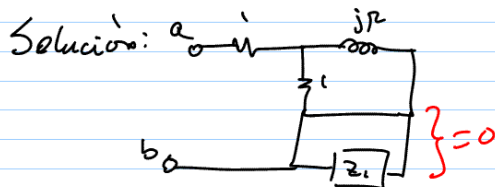


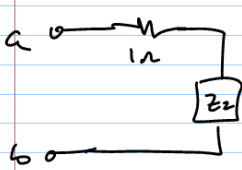
$$z_2 = \frac{j}{1+j} \left(\frac{1-j}{1-j} \right) = \frac{j-j^2}{1-j^2} = \frac{1+j}{2}$$


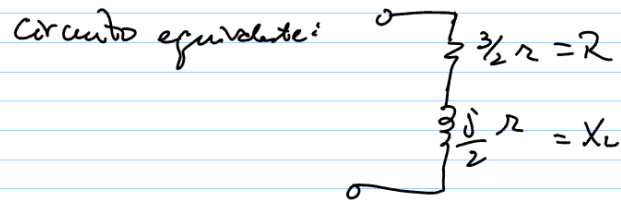
$$z_{ab} = z_2 + 1 = \frac{1}{2} + \frac{j}{2} + 1 = \frac{3}{2} + \frac{j}{2} = z_{ab}$$



Ejemplo: Evaluar z_{ab}

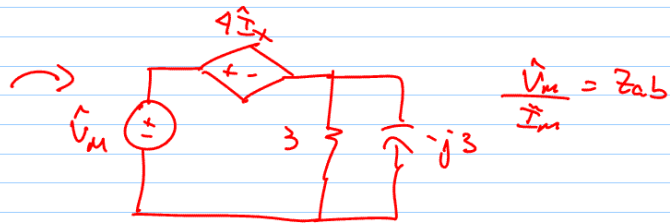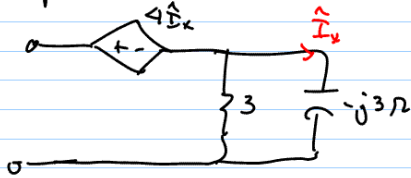

$$\text{KCL: } \hat{I}_m - \hat{I}_3 - \hat{I}_x = 0 \quad ; \quad \hat{I}_3 = \frac{\hat{V}_3}{3\Omega} \quad ; \quad \hat{I}_x = \frac{\hat{V}_3}{-3j}$$


$$\text{análisis: KVL: } \hat{V}_m - 4\hat{I}_x - \hat{V}_3 = 0 \quad ; \quad \hat{I}_m = \frac{\hat{V}_3}{3} + \frac{\hat{V}_3}{-3j} \quad ;$$

$$\hat{V}_3 = \frac{\hat{I}_m}{\frac{1}{3} - \frac{1}{3j}}$$


$$\hat{V}_m = 4\left(\frac{\hat{V}_3}{-3j}\right) + \hat{V}_3 = \hat{V}_3 \left(1 - \frac{4}{3j}\right) \quad ; \quad \hat{V}_3 = \frac{\hat{V}_m}{1 - \frac{4}{3j}}$$

$$\frac{\hat{V}_m}{\hat{I}_m} = z_{ab} = \frac{\left(1 - \frac{4}{3j}\right)}{\left(\frac{1}{3} - \frac{1}{3j}\right)} = \frac{3 - 4j}{1 - j} = \dots = \frac{7}{2} + \frac{j}{2}$$

Circuito equivalente:

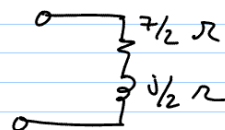

Exemplo: Evolucaõ de dados:


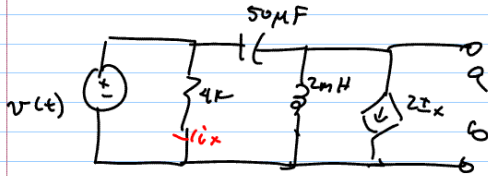


$$v(t) = 16 \cos(377t + 45^\circ) \text{ V}$$


$$f = ? \quad \omega = 377 = 2\pi f \quad ; \quad f = 60 \text{ Hz}$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{377(50\mu\text{F})} = -j53 \Omega$$

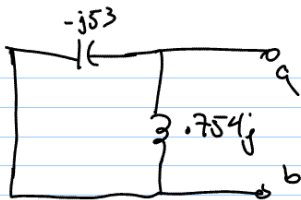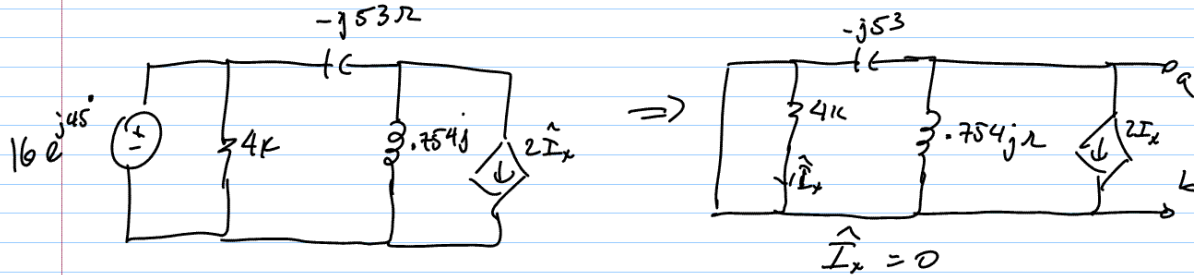
$$Z_L = j\omega L = j(377)(2 \times 10^{-3}) = .754 j$$


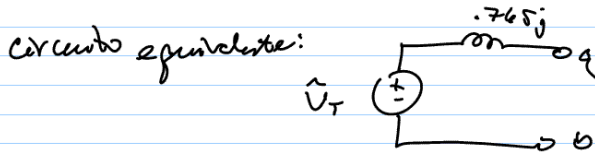
$$Z_{ab} = \frac{-53j (.754j)}{-53j + .754j} \Omega = j .765 \Omega$$



Exemplo: Avalie \hat{V}_0 .

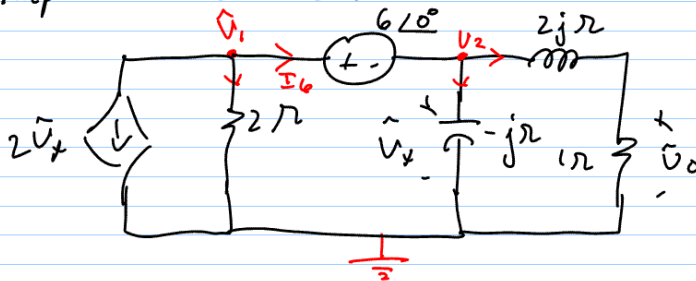

ANÁLISE POR NÓS:

Solution: KCL @ \hat{V}_1 : $2\hat{V}_x + \frac{\hat{V}_1}{2} + I_G = 0$

KCL @ \hat{V}_2 : $I_G - \frac{\hat{V}_2}{-j\Omega} - \frac{\hat{V}_2}{1+j2\Omega} = 0$

controls: $\hat{V}_x = V_2$; $\hat{V}_1 - \hat{V}_2 = 6 \angle 0^\circ = 6e^{j0}$

$$\hat{V}_0 = \frac{V_2}{1+2j} \cdot 1\Omega$$

Going back to KCL @ \hat{V}_1 : $2\hat{V}_2 + \frac{\hat{V}_1}{2} + \frac{\hat{V}_2}{-j} + \frac{\hat{V}_2}{1+2j} = 0$

re-writing: $\hat{V}_2 \left(2 + \frac{1}{-j} + \frac{1}{1+2j} \right) = -\frac{1}{2}(\hat{V}_2 + 6)$

$$\hat{V}_2 \left[2 + j + \frac{1}{1+2j} \right] = -\frac{1}{2}(\hat{V}_2 + 6)$$


$$\hat{V}_2 \left[2 + j + \frac{1}{2+j} \right] = -3 ; \quad \hat{V}_2 = \frac{-3}{\frac{5}{2} + j + \frac{1}{2+j}} = \frac{-3}{\frac{5}{2} + j + \frac{1-2j}{5}} = \frac{-3}{2.7 + 0.6j}$$

$$\hat{V}_0 = \frac{-3}{\frac{2.7 + 0.6j}{1+2j}} = \frac{-3}{(1+2j)(2.7 + 0.6j)} = \frac{-3}{(2.7 + 0.6j + 5.4j - 1.2)}$$

$$\hat{V}_0 = \frac{-3}{1.5 + 6j} = \frac{-3(1.5 - 6j)}{2.25 + 36} = \frac{-4.5 + 18j}{38.25} ;$$

$$\hat{V}_0 = -.11 + .47j = .48 \angle 104^\circ \text{ V}$$

Obtaining:
Evaluate \hat{V}_0 :

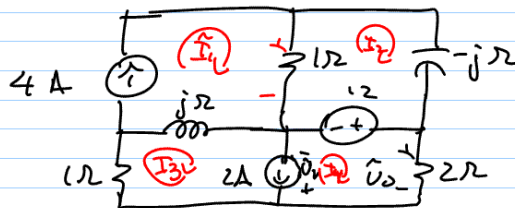

Método: Mallas. $\hat{I}_1 = 4A$

$$\text{KVL @ } \hat{I}_2; \quad 12(\hat{I}_1 - \hat{I}_2) - \hat{I}_2(-j2) - 12 = 0$$

$$\hat{I}_1(12) + \hat{I}_2(-1+j2) = 12; \quad \hat{I}_2 = \frac{12-4}{-1+j2} = \frac{8}{-1+j2}$$

$$\hat{I}_2 = \frac{8}{-1+j2} \frac{(-1-j2)}{(-1-j2)} = \frac{-8-8j}{1+1} = \frac{-8-8j}{2} = -4-4j = \hat{I}_2$$

~~KVL @ I_3~~
Suma de voltajes
f.e. de RL

$$1\Omega(I_3) + 0 - \hat{V}_2 = -j(\hat{I}_3 - 4A)$$

$$\text{KVL @ } \hat{I}_4: \hat{I}_4(2) - 12 + \hat{V}_2 = 0; \quad \text{auxiliares:}$$

$$\hat{I}_3 - \hat{I}_4 = 2A$$

$$\hat{V}_2 = 2\hat{I}_4$$

$$\text{Reemplazando } \hat{I}_3(1+j) - j4 = 12 - 2\hat{I}_4$$

$$(2 + \hat{I}_4)(1+j) - 4j + 2\hat{I}_4 = 12$$

$$(2+2j) + I_4(1+j+2) = 12+j4$$

$$\hat{I}_4 = \frac{10+j2}{3+j} = \frac{(10+j2)(3-j)}{10} = \frac{30+6j-10j+2}{10}$$

$$= \frac{32-4j}{10} = 3.2 - .4j = 3.22 \angle -7.12^\circ A$$

$$\hat{V}_2 = 6.44 \angle -7.12^\circ V$$

