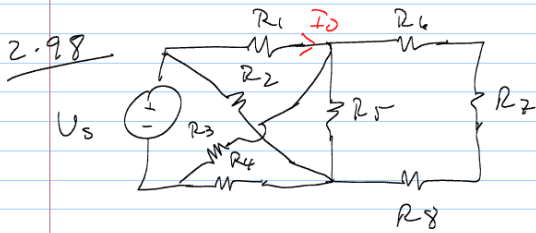



INEL 3105 Lecture 6.0 (ejercicios de práctica)

Note Title

8/28/2009

Hallar I_0 .

Primer paso: Reducir el circuito:

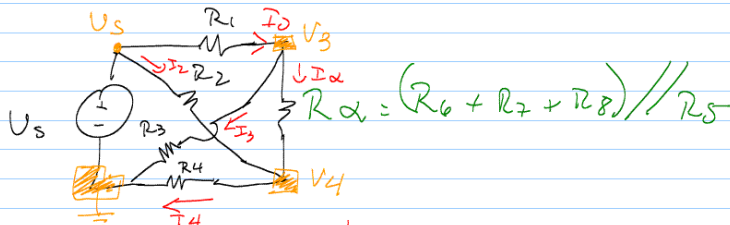

Segundo paso: Análisis de nodos

Step 1: Identificar ϕ Step 2: Label all voltajes

Step 3: Write KCL's

KCL @ V_3

$$I_0 - \frac{V_3}{R_3} - \left(\frac{V_3 - V_4}{R_\alpha} \right) = 0$$

KCL @ V_4 :

$$\left(\frac{V_3 - V_4}{R_\alpha} \right) + \frac{V_3 - V_4}{R_2} - \frac{V_4}{R_4} = 0$$

$$I_0 = \frac{V_s - V_3}{R_1}$$

Combinando términos:

$$V_3 \left(\frac{-1}{R_3} - \frac{1}{R_\alpha} - \frac{1}{R_1} \right) + V_4 \left(\frac{1}{R_\alpha} \right) = \frac{-V_s}{R_1}$$

$$V_3 \left(\frac{1}{R_\alpha} \right) + V_4 \left(\frac{-1}{R_\alpha} - \frac{1}{R_2} - \frac{1}{R_4} \right) = \frac{-V_s}{R_2}$$

Step 4: En forma de matriz:

$$\begin{bmatrix} \frac{-1}{R_3} & -\frac{1}{R_\alpha} & -\frac{1}{R_1} & \frac{1}{R_\alpha} \\ \frac{1}{R_\alpha} & -\frac{1}{R_\alpha} & -\frac{1}{R_2} & -\frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} \frac{-V_s}{R_1} \\ \frac{-V_s}{R_2} \end{bmatrix}$$

$R_2 = 6\Omega$; $V_s = 36V$, $R_1 = 2\Omega$, $R_2 = 9\Omega$, $R_3 = 12\Omega$, $R_4 = 18\Omega$


$$\frac{-3}{4} \begin{bmatrix} \frac{-1}{12} & \frac{-1}{6} & \frac{-1}{2} & 0 \\ \frac{1}{6} & \frac{-1}{6} & \frac{-1}{9} & \frac{-1}{18} \end{bmatrix} \begin{bmatrix} U_3 \\ U_4 \end{bmatrix} = \begin{bmatrix} -18 \\ -4 \end{bmatrix}$$

$\frac{1}{3}$

$U_3 = 30$
 $U_4 = 27$

Equation auxiliar: $I_o = \frac{V_s - U_3}{R_1} = \frac{36 - 30}{2} = \frac{6}{2} = 3A$

2.57

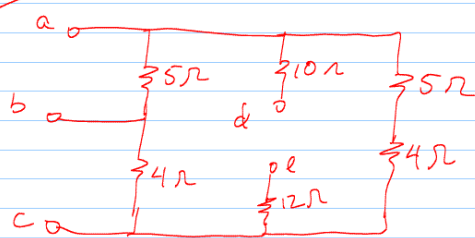

$R_{ab} = 5 \parallel (5 + 4 + 4) =$


$R_{bc} = 4 \parallel (5 + 4 + 5) =$

$R_{ac} = (5 + 4) \parallel (5 + 4) =$


$R_{de} = [(5 + 4) \parallel (5 + 4)] + 10 + 12 =$


$R_{ae} = [(5 + 4) \parallel (5 + 4)] + 12 =$

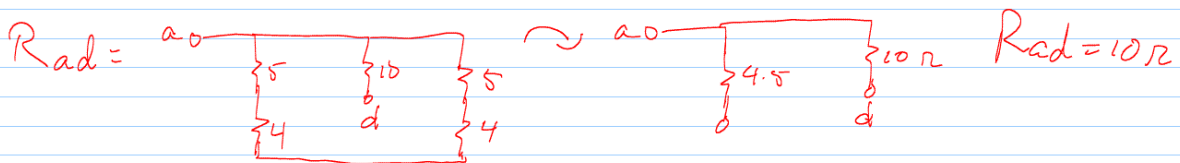$R_{cd} = [(5 + 4) \parallel (5 + 4)] + 10 =$



3.94

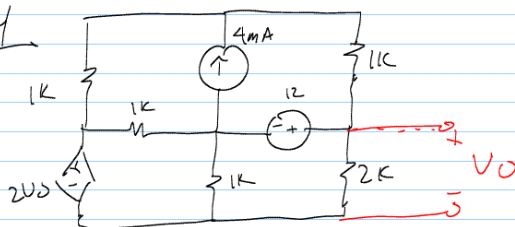

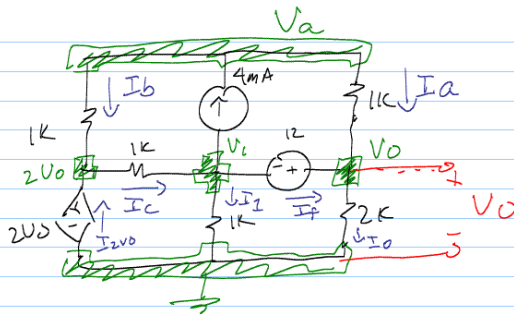

Analysis by nodes:

Step 1: Identify nodes

Step 2: Label all voltages.

Step 3: Write KCL's

$$\text{KCL @ } V_a: 4\text{mA} - \left(\frac{V_a - V_o}{1\text{k}}\right) - \left(\frac{V_a - 2V_o}{1\text{k}}\right) = 0$$

$$\text{KCL @ } V_i: -4\text{mA} - I_f - \frac{V_i}{1\text{k}} + \left(\frac{2V_o - V_i}{1\text{k}}\right) = 0$$

$$\text{KCL @ } 2V_o: \left(\frac{V_a - 2V_o}{1\text{k}}\right) + I_{2V_o} - \left(\frac{2V_o - V_i}{1\text{k}}\right) = 0$$

5 variables; 3 equations;

Equaciones auxiliares:

$$1. V_o - V_i = 12; V_i = V_o - 12$$

$$2. \frac{V_o}{2\text{k}} + \frac{V_i}{1\text{k}} = I_{2V_o} = \frac{V_o}{2\text{k}} + \frac{V_o - 12}{1\text{k}} = V_o \left(\frac{1}{2\text{k}} + \frac{1}{1\text{k}}\right) - \frac{12}{1\text{k}}$$

$$I_{2V_o} = V_o \left(\frac{3}{2\text{k}}\right) - \frac{12}{1\text{k}}$$

Re-write KCL's:

$$V_a: -\left(\frac{V_a - V_o}{1\text{k}}\right) - \left(\frac{V_a - 2V_o}{1\text{k}}\right) = -4\text{mA}$$

$$V_i: -I_f - \left(\frac{V_o - 12}{1\text{k}}\right) + \left(\frac{2V_o}{1\text{k}}\right) - \left(\frac{V_o - 12}{1\text{k}}\right) = 4\text{mA}$$

$$2V_o: \left(\frac{V_a - 2V_o}{1\text{k}}\right) + V_o \left(\frac{3}{2\text{k}}\right) - \left(\frac{2V_o - (V_o - 12)}{1\text{k}}\right) = \frac{12}{1\text{k}}$$

3 equations, 3 desconocidos

Combining terms:

$$V_a: V_a \left(\frac{-1}{1\text{k}} - \frac{1}{1\text{k}}\right) + V_o \left(\frac{1}{1\text{k}} + \frac{2}{1\text{k}}\right) + I_f(0) = -4\text{mA}$$

$$V_i: V_a(0) + V_o \left(\frac{2}{1\text{k}} - \frac{1}{1\text{k}} - \frac{1}{1\text{k}}\right) + I_f(-1) = -20\text{mA}$$

$$2V_o: V_a \left(\frac{1}{1\text{k}}\right) + V_o \left(\frac{3}{2\text{k}} - \frac{2}{1\text{k}} - \frac{1}{1\text{k}}\right) + I_f(0) = \frac{12}{1\text{k}}$$

In matrix form

$$\begin{bmatrix} \frac{-1}{2k} & \frac{3}{1k} & 0 \\ 0 & 0 & -1 \\ \frac{1}{1k} & \frac{-3}{2k} & 0 \end{bmatrix} \begin{bmatrix} V_a \\ V_o \\ I_f \end{bmatrix} = \begin{bmatrix} -4mA \\ -20mA \\ \frac{12}{1k} \end{bmatrix}$$

$$V_a = 13.33 ; V_o = 0.888 V ;$$

$$I_f = 20mA$$

El solucionario dice que el sistema no tiene solución ... ¿dónde está el error?