Chapter 4 – Methods of Analysis of Resistive Circuits

Exercises

Ex 4.3-1

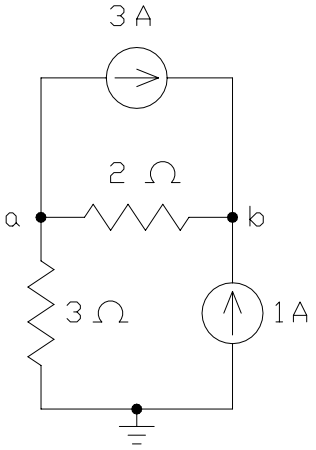

KCL at a: $\frac{v_a}{3}+\frac{v_a-v_b}{2}+3=0 \quad \Rightarrow \quad 5\,v_a-3\,v_b=-18$

KCL at b: $\frac{v_b-v_a}{2}-3-1=0 \quad \Rightarrow \quad v_b-v_a=8$

Solving these equations gives:

$v_a = 3$ V and $v_b = 11$ V

Ex 4.3-2

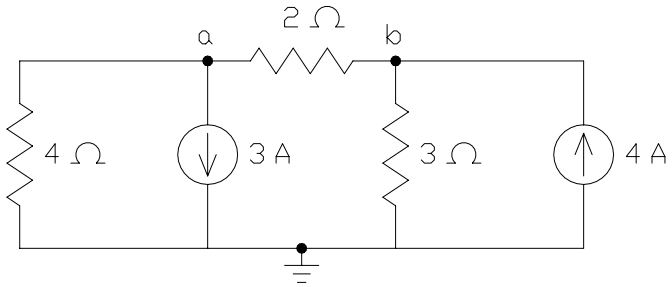

KCL at a:

$$\frac{v_a}{4}+\frac{v_a-v_b}{2}+3=0 \quad \Rightarrow \quad 3\,v_a-2\,v_b=-12$$

KCL at a:

$$\frac{v_b}{3}-\frac{v_a-v_b}{2}-4=0 \quad \Rightarrow \quad -3\,v_a+5\,v_b=24$$

Solving:

v_a = -4/3 V and v_b = 4 V

Ex. 4.4-1 $2+\frac{v_b+10}{20}+\frac{v_b}{30}=5 \quad \Rightarrow \quad v_b=30$ V and $v_a=40$ V

Ex. 4.4-2 $\frac{(v_b+8)-(-12)}{10}+\frac{v_b}{40}=3 \quad \Rightarrow \quad v_b=8$ V and $v_a=16$ V

Ex 4.5-1 Apply KCL at node a to express i_a as a function of the node voltages. Substitute the result into $v_b=4\,i_a$ and solve for v_b.

$$v_b=4\left(\frac{9+v_b}{12}\right) \quad \Rightarrow \quad v_b=4.5 \text{ V}$$

Ex. 4.5-2 : The controlling voltage of the dependent source is a node voltage so it is already expressed as a function of the node voltages. Apply KCL ate node a.

$$\frac{v_a - 6}{20} + \frac{v_a - 4\,v_a}{15} = 0 \quad \Rightarrow \quad v_a = -2 \text{ V}$$

Ex. 4.6-1

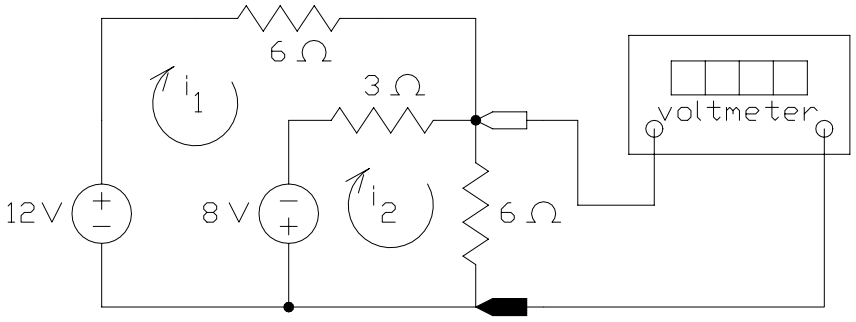

Mesh equations:

$$-12 + 6\,i_1 + 3\left(i_1 - i_2\right) - 8 = 0 \quad \Rightarrow \quad 9\,i_1 - 3\,i_2 = 20$$

$$8 - 3\left(i_1 - i_2\right) + 6\,i_2 = 0 \quad \Rightarrow \quad -3\,i_1 + 9\,i_2 = -8$$

Solving these equations gives:

$$i_1 = \frac{13}{6} \text{ A} \text{ and } i_2 = -\frac{1}{6} \text{ A}$$

The voltage measured by the meter is 6 i_2 = -1 V.

Ex 4.7-1

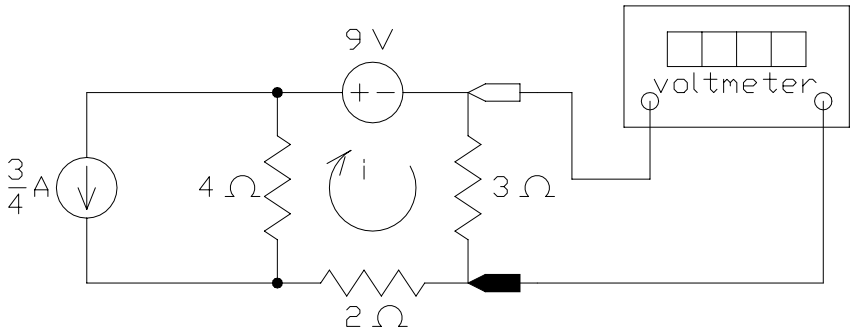

Mesh equation: $9 + 3\,i + 2\,i + 4\left(i + \frac{3}{4}\right) = 0 \quad \Rightarrow \quad (3+2+4)\,i = -9 - 3 \quad \Rightarrow \quad i = \frac{-12}{9} \text{ A}$

The voltmeter measures $3\,i = -4$ V

Ex 4.7-2

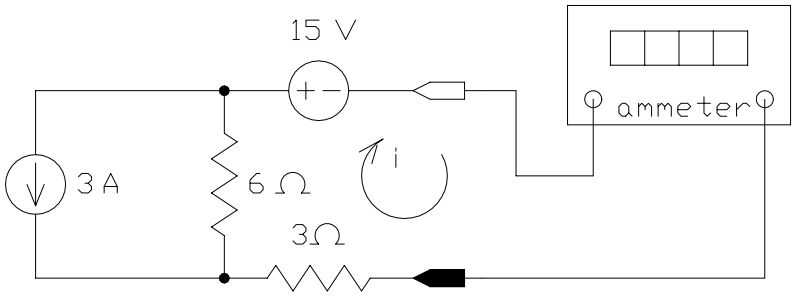

Mesh equation: $15+3i+6(i+3)=0 \;\Rightarrow\; (3+6)i=-15-6(3) \;\Rightarrow\; i=\frac{-33}{9}=-6\frac{2}{3}$ A

Ex 4.7-3

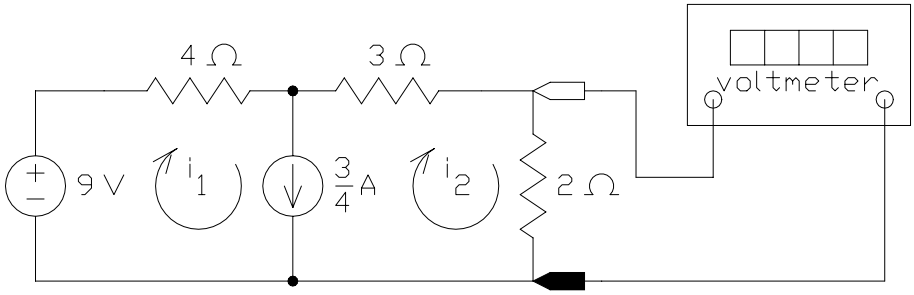

Express the current source current in terms of the mesh currents: $\frac{3}{4}=i_1-i_2 \;\Rightarrow\; i_1=\frac{3}{4}+i_2.$

Apply KVL to the supermesh: $-9+4i_1+3i_2+2i_2=0 \;\Rightarrow\; 4\left(\frac{3}{4}+i_2\right)+5i_2=9 \;\Rightarrow\; 9i_2=6$

so $i_2=\frac{2}{3}$ A and the voltmeter reading is $2i_2=\frac{4}{3}$ V

Ex 4.7-4

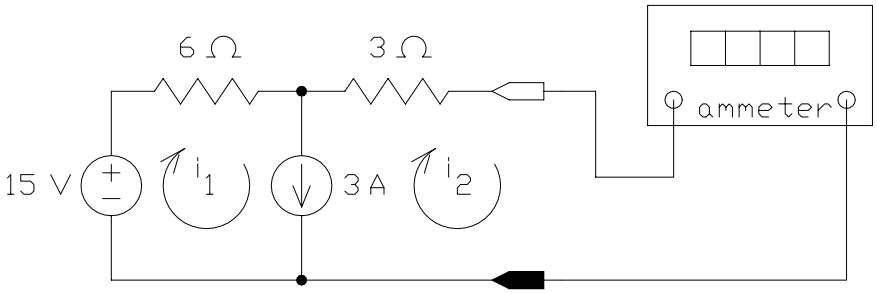

Express the current source current in terms of the mesh currents: $3=i_1-i_2 \;\Rightarrow\; i_1=3+i_2.$

Apply KVL to the supermesh: $-15+6i_1+3i_2=0 \;\Rightarrow\; 6(3+i_2)+3i_2=15 \;\Rightarrow\; 9i_2=-3$

Finally, $i_2=-\frac{1}{3}$ A is the current measured by the ammeter.

Ex. 4.7-5

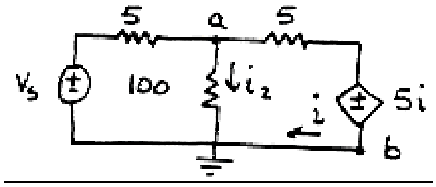

$v_{ab} = 5i + 5i = 10i$

$\therefore P_{motor} = (v_{ab})i = 10i^2 = 150$

$\Rightarrow i = \sqrt{15}$ A

$\therefore v_{ab} = (10)(\sqrt{15})$ V

$\Rightarrow i_2 = \dfrac{v_{ab}}{100} = \dfrac{\sqrt{15}}{10}$ A

KCL at a : $\dfrac{(v_{ab} - v_s)}{5} + i_2 + i = 0 \quad \Rightarrow \quad v_s = \dfrac{31}{2}\sqrt{15} = 60.03$ V

Ex. 4.7-6

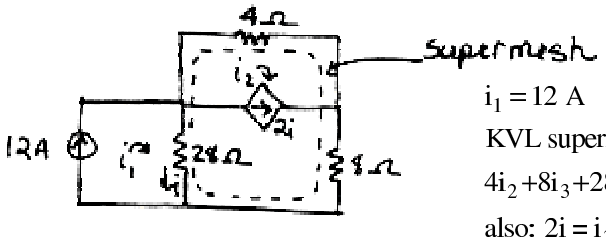

$i_1 = 12$ A (1)

KVL supermesh:

$4i_2 + 8i_3 + 28(i_3 - 12) = 0$ (2)

also: $2i = i_3 - i_2$ (3)

Solving $(1) \rightarrow (3)$ yields $i_3 = 9$A

$\therefore i = 12 - 9 = 3$ A

Ex. 4.8-1

(a) Nodal analysis since the other node is known (= v_s);
thus only need one node equation at a.

(b) Nodal analysis since when the circuit is redrawn
(shown below), only one node equation at v_a is required

Mesh analysis would require
4 mesh currents
$\Rightarrow$ 4 unknows.

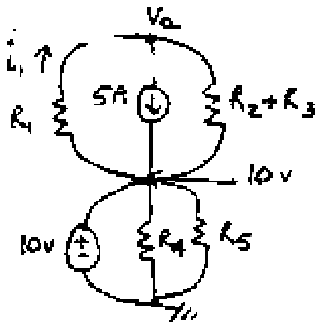

Problems

Section 4-3 Node Voltage Analysis of Circuits with Current Sources

P4.3-1

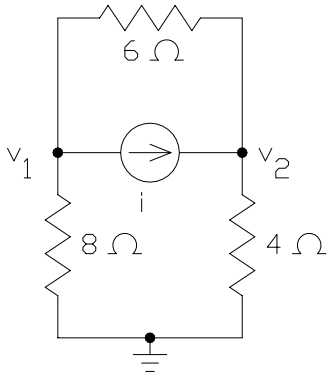

KCL at node 1:

$$0=\frac{v_1}{8}+\frac{v_1-v_2}{6}+i=\frac{-4}{8}+\frac{-4-2}{6}+i=-1.5+i \quad \Rightarrow \quad i=1.5 \text{ A}$$

P 4.3-2

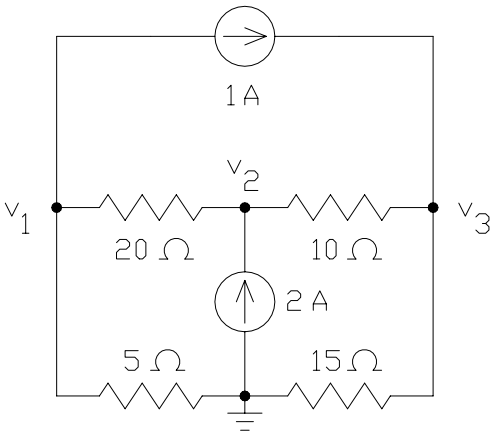

KCL at node 1:

$$\frac{v_1-v_2}{20}+\frac{v_1}{5}+1=0 \quad \Rightarrow \quad 5v_1-v_2=-20$$

KCL at node 2:

$$\frac{v_1-v_2}{20}+2=\frac{v_2-v_3}{10} \quad \Rightarrow \quad -v_1+3v_2-2v_3=40$$

KCL at node 3:

$$\frac{v_2-v_3}{10}+1=\frac{v_3}{15} \quad \Rightarrow \quad -3v_2+5v_3=30$$

Solving gives $v_1 = 2$ V, $v_2 = 30$ V and $v_3 = 24$ V.

P 4.3-3

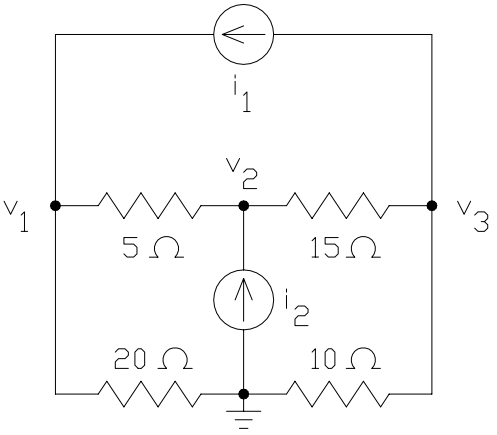

KCL at node 1:

$$\frac{v_1-v_2}{5}+\frac{v_1}{20}=i_1 \quad \Rightarrow \quad i_1=\frac{4-15}{5}+\frac{4}{20}=-2 \text{ A}$$

KCL at node 2:

$$\frac{v_1-v_2}{5}+i_2=\frac{v_2-v_3}{15} \quad \Rightarrow \quad i_2=-\left(\frac{4-15}{5}\right)+\frac{15-18}{15}=2 \text{ A}$$

P4.3-4

$$-.003+\frac{v_1}{R_1}+\frac{v_1-v_2}{500}=0$$

$$-\frac{v_1-v_2}{500}+\frac{v_2}{R_2}-.005=0$$

When

$v_1 = 1$ and $v_2 = 2$

$$-.003+\frac{1}{R_1}+\frac{-1}{500}=0\Rightarrow R_1=\frac{1}{.003+\frac{1}{500}}=\underline{200\Omega}$$

$$-\frac{-1}{500}+\frac{2}{R_2}-.005=0\Rightarrow R_2=\frac{2}{.005-\frac{1}{500}}=\underline{667\Omega}$$

P 4.3-5

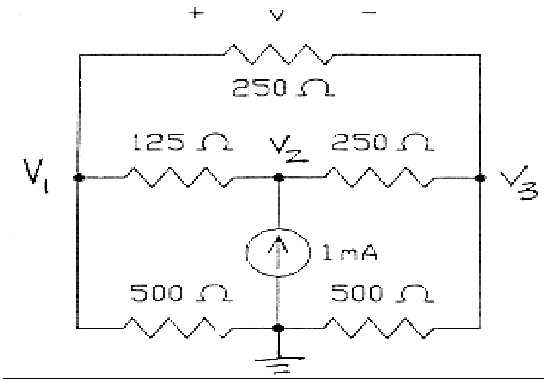

$$\frac{v_1}{500}+\frac{v_1-v_2}{125}+\frac{v_1-v_3}{250}=0$$

$$-\frac{v_1-v_2}{125}-.001+\frac{v_2-v_3}{250}=0$$

$$-\frac{v_2-v_3}{250}-\frac{v_1-v_3}{250}+\frac{v_3}{500}=0$$

$\Rightarrow v_1 = 0.261$ V

$v_2 = 0.337$ V

$v_3 = 0.239$ V

Finally, $v = v_1 - v_3 = \underline{0.022\text{ V}}$

Section 4-4 Node Voltage Analysis of Circuits with Current and Voltage Sources

P4.4-1

$$\frac{v_a-10}{100}+\frac{v_a}{100}+\frac{v_a-2}{100}=0\Rightarrow 3v_a=12$$

$$\Rightarrow \underline{v_a = 4\text{ V}}$$

P4.4-2

$$-.003+\frac{v_a+8}{500}+\frac{v_a}{500}-.005=0$$

$$\therefore \underline{v_a=-2\text{ V}}$$

P4.4-3

$$\frac{v_a-10}{100}+\frac{v_a}{100}+\frac{v_a-8}{100}-.03=0$$

$$\therefore \underline{v_a=7\text{ V}}$$

P4.4-4

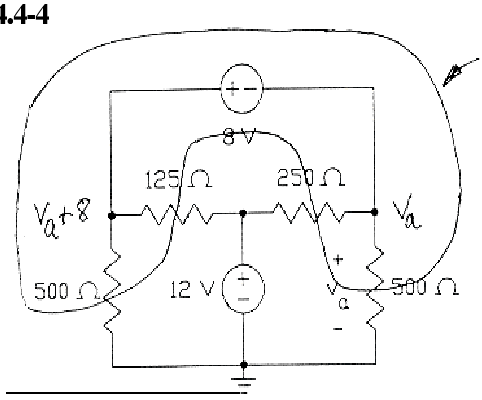

$$\frac{v_a+8}{500}+\frac{(v_a+8)-12}{125}+\frac{v_a-12}{250}+\frac{v_a}{500}=0$$

$$\therefore \underline{v_a=4\text{ V}}$$

P4.4-5

$$-\frac{10-6}{100}+\frac{6}{R_3}+\frac{6-4}{100}=0 \Rightarrow \underline{R_3 = 300\Omega}$$

P4.4-6

a)

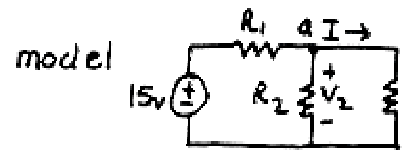

need to keep v_2 across R_2 as $4.8 \le v_2 \le 5.4$

I=.3 or .1 A depending on whether activated or not

↑ ↑

display is not

active active

KCL at a: $\frac{v_2-15}{R_1}+\frac{v_2}{R_2}+I=0$

$\Rightarrow v_2' = 4.8\text{v}$ ($I' = .3\text{A}$) & $v_2'' = 5.4\text{V}$ ($I''=.1\text{A}$)

assumed that maximum I results in minimum v_2 and Visa-Versa

Now plug in v_2' & v_2' into KCL eqn. to generate 2 eqns and then solve for R_1 & $R_2 \Rightarrow \underline{R_1 = 7.89\ \Omega}$, $\underline{R_2 = 4.83\ \Omega}$

b) $I_{R_{1max}} = \frac{15-4.8}{7.89} = 1.292\text{ A} \Rightarrow P_{R_{1max}} = (1.292)^2(7.89) = 13.17\text{ W}$

$I_{R_{2max}} = \frac{5.4}{4.83} = 1.118\text{ A} \Rightarrow P_{R_{2max}} = \frac{(5.4)^2}{4.83} = 6.03\text{ W}$

$I_{15v_{max}} = 1.292\text{ A}$

c) No; if the supply voltage (15V) were to rise or drop, the voltage at the display would drop below 4.8V or rise above 5.4V. The power dissipated in the resistors is excessive. Most of the power from the supply is dissipated in the resistors, not the display.

P4.4-7 Label the voltage measured by the meter. Notice that this is a node voltage.

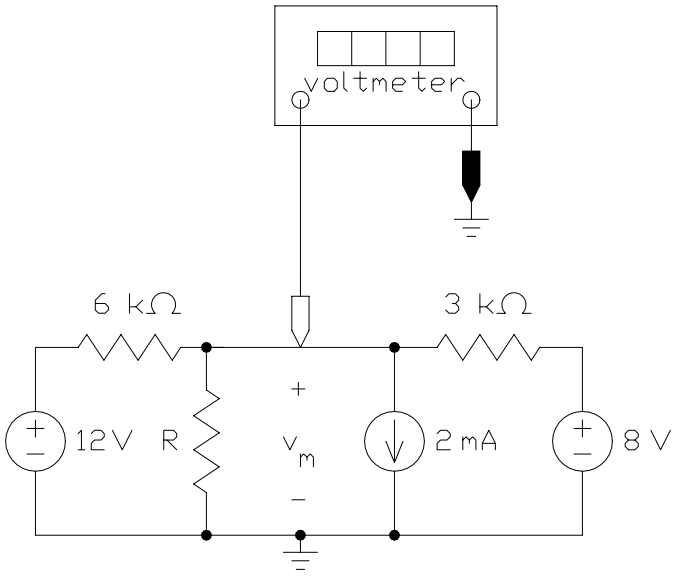

Write a node equation at the node at which the node voltage is measured.

$$-\left(\frac{12-v_m}{6\,\text{k}\Omega}\right)+\frac{v_m}{R}+2\,\text{mA}+\frac{v_m-8}{3\,\text{k}\Omega}=0$$

That is

$$\left(3+\frac{6\,\text{k}\Omega}{R}\right)v_m=16 \;\Rightarrow\; R=\frac{6\,\text{k}\Omega}{\dfrac{16}{v_m}-3}$$

(a) The voltage measured by the meter will be 4 volts when R = 6 kΩ.
(b) The voltage measured by the meter will be 2 volts when R = 1.2 k Ω.

P4.4-8

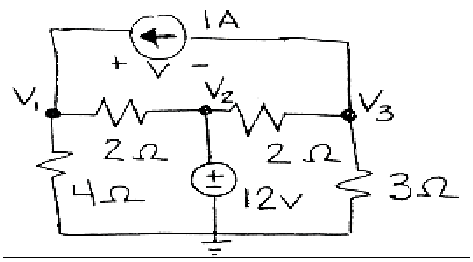

$v = v_1 - v_3$
$v_2 = 12$ V

KCL at v_1: $\frac{v_1}{4} + \frac{v_1 - v_2}{2} - 1 = 0$

KCL at v_3: $\frac{v_3}{3} + \frac{v_3 - v_2}{2} + 1 = 0$

Solving for v_1 & v_3 : $v_1 = 9.33$ V

$v_3 = 6$ V

$v = 9.33 - 6 = \underline{3.33\text{ V}}$

Section 4-5 Node Voltage Analysis with Dependent Sources

P4.5-1

$$v_a = 9 - v_b - \frac{9 - v_b}{100} + (.02)(9 - v_b) + \frac{v_b}{200} = 0$$

$$\therefore \ \underline{v_b = +18\ V};\ v_a = -9\ \text{V}$$

P4.5-2

$$-.002 + \frac{v_a}{10{,}000} + \frac{v_a - 4000\left(\frac{v_a}{10{,}000}\right)}{6000} = 0$$

$$-.002 + \frac{v_a}{10{,}000} + \frac{.6v_a}{6000} = 0 \Rightarrow \underline{v_a = 10\ \text{V}}$$

P4.5-3

$$\frac{v_a - 6}{1000} + \frac{v_a}{2000} + \frac{v_a - 4v_a}{3000} = 0 \Rightarrow v_a = 12\ \text{V}$$

$$i_b = \frac{v_a - 4v_a}{3000} = \underline{-12\ \text{mA}}$$

P4.5-4

$$i_a = \frac{2 - v_b}{4000}$$

$$-\frac{2 - v_b}{4000} + \frac{v_b}{2000} - 5\left(\frac{2 - v_b}{4000}\right) = 0 \Rightarrow \underline{v_b = 1.5\ \text{V}}$$

P 4.5-5

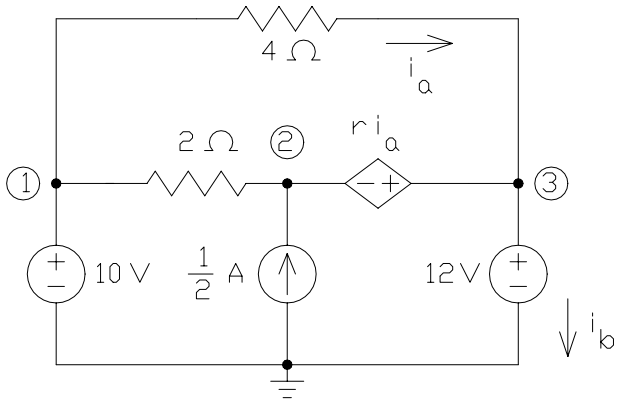

Apply KCL to the supernode of the CCVS to get

$$\frac{12 - 10}{4} + \frac{14 - 10}{2} - \frac{1}{2} + i_b = 0 \Rightarrow i_b = -2\ \text{A}$$

Next

$$\left.\begin{aligned} i_a &= \frac{10 - 12}{4} = -\frac{1}{2} \\ r\,i_a &= 12 - 14 \end{aligned}\right\} \Rightarrow r = \frac{-2}{-\frac{1}{2}} = 4\ \frac{\text{V}}{\text{A}}$$

P4.5-6

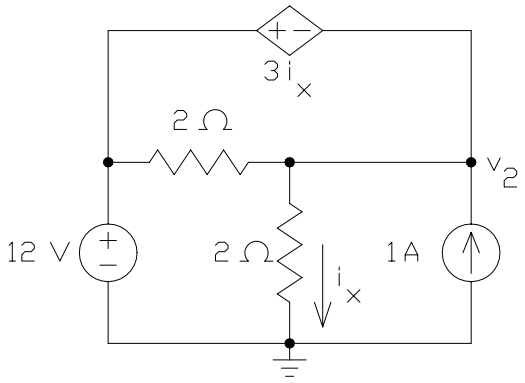

First, express the controlling current of the CCVS in terms of the node voltages: $i_x = \dfrac{v_2}{2}$

Next, express the controlled voltage in terms of the node voltages:

$$12 - v_2 = 3i_x = 3\frac{v_2}{2} \quad \Rightarrow v_2 = \frac{24}{5}\ \text{V}$$

so i_x = 12/5 A = 2.4 A.

P4.5-7

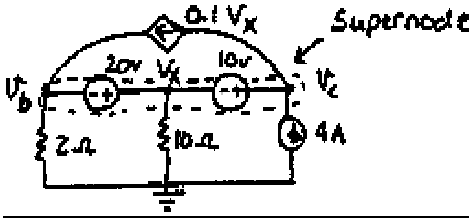

KCL: $\frac{v_b}{2} + \frac{v_x}{10} + 4 = 0$ (1)

also $v_b = v_x - 20$ (2)

(1) & (2) yields $v_x = 10$ V

Section 4-6 Mesh Current Analysis with Independent Voltage Sources

P 4.6-1

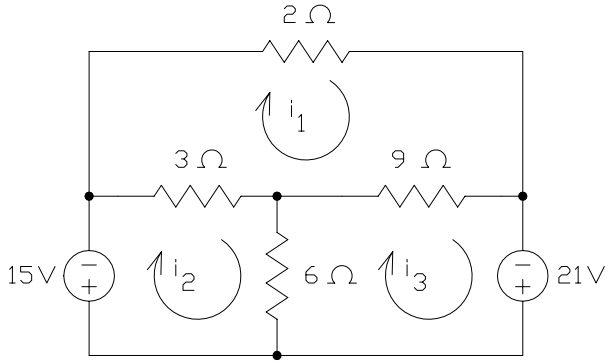

$$2i_1 + 9(i_1 - i_3) + 3(i_1 - i_2) = 0$$
$$15 - 3(i_1 - i_2) + 6(i_2 - i_3) = 0$$
$$-6(i_2 - i_3) - 9(i_1 - i_3) - 21 = 0$$

or

$$14i_1 - 3i_2 - 9i_3 = 0$$
$$-3i_1 + 9i_2 - 6i_3 = -15$$
$$-9i_1 - 6i_2 + 15i_3 = 21$$

so

i_1 = 3 A, i_2 = 2 A and i_3 = 4 A.

P 4.6-2

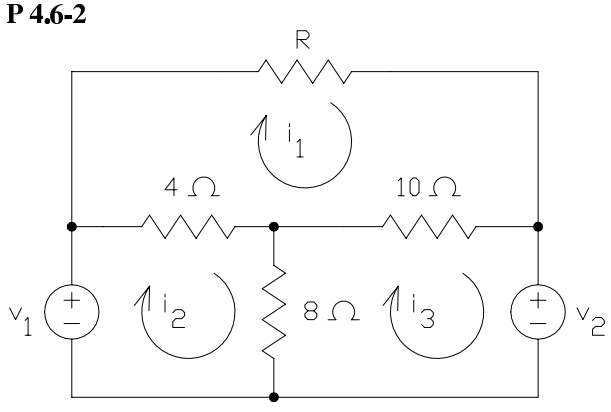

Top mesh:

$$4(2-4) + R(2) + 10(2-4) = 0$$

so R = 12 Ω.

Bottom, left mesh:

$$8(4-3) + 10(4-2) + v_2 = 0$$

so v_2 = -28 V.

Bottom right mesh

$$-v_1 + 4(3-2) + 8(3-4) = 0$$

so v_1 = -4 V.

P4.6-3

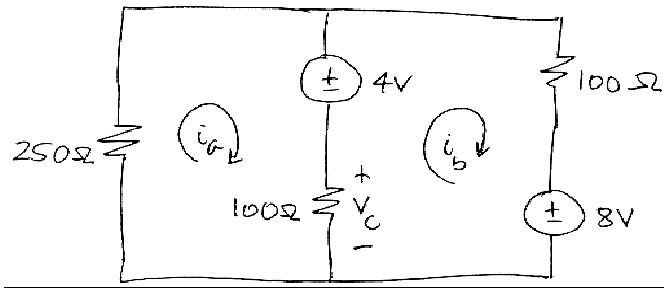

loop a $\quad 250\ i_a + 4 + 100\,(i_a - i_b) = 0$

$\quad 350\ i_a - 100\, i_b = -4$

loop b $\quad -100(i_a - i_b) - 4 + 100\, i_b + 8 = 0$

$\quad -100\, i_a + 200\, i_b = -4$

$\quad \underline{i_a = -20\ \text{mA}}\ ,\ \underline{i_b = -30\ \text{mA}}$

P4.6-4

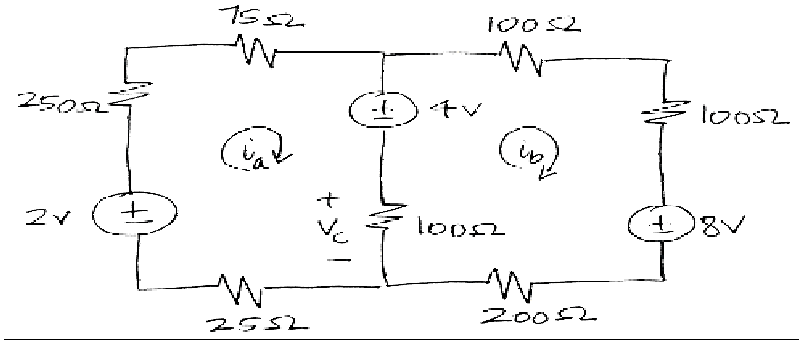

loop 1 $\quad 25\, i_a - 2 + 250\, i_a + 75\, i_a + 4 + 100\,(i_a - i_b) = 0$

$\quad 450\, i_a - 100\, i_b = -2$

loop2 $\quad -100(i_a - i_b) - 4 + 100\, i_b + 100\, i_b + 8 + 200\, i_b = 0$

$\quad -100\, i_a + 500\, i_b = -4$

$\quad \underline{i_a = -6.5\ \text{mA}}\ ,\ \underline{i_b = -9.3\ \text{mA}}$

P4.6-5

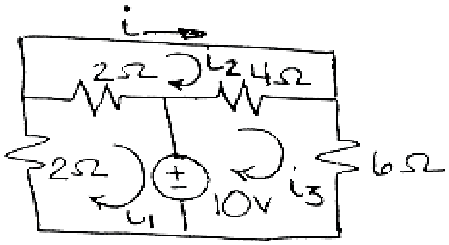

KVL1 : $\quad 2i_1 + 2\,(i_1 - i_2) + 10 = 0$

KVL2 : $2(i_2 - i_1) + 4\,(i_2 - i_3) = 0$

KVL3 : $\quad -10 + 4\ (i_3 - i_2) + 6\, i_3 = 0$

$i = i_2 \Rightarrow \underline{i = -0.294\ \text{A}}$

Section 4-7 Mesh Current Analysis with Voltage and Current Sources

(a) Independent Sources

P4.7-1

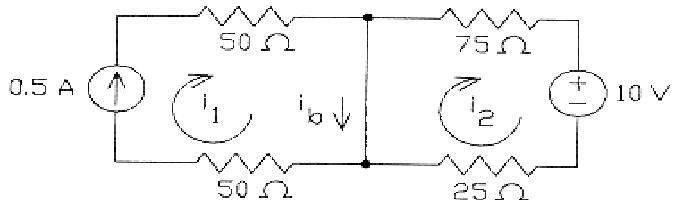

loop 1 $\quad i_1 = \frac{1}{2}$ A

loop 2 $\quad 75\,i_2 + 10 + 25\,i_2 = 0 \Rightarrow i_2 = -0.1$ A

$i_b = i_1 - i_2 = \underline{0.6\text{ A}}$

P4.7-2

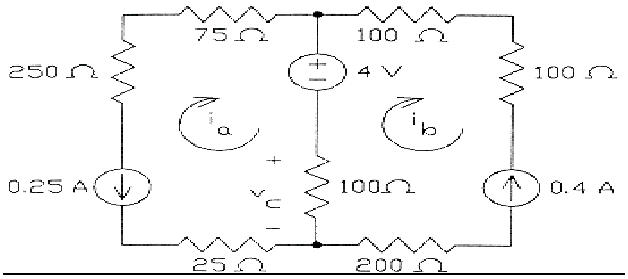

loop a $\quad i_a = -0.25$ A

loop b $\quad i_b = -0.4$ A

$v_c = 100(i_a - i_b) = 100(0.15) = \underline{15\text{ V}}$

P4.7-3

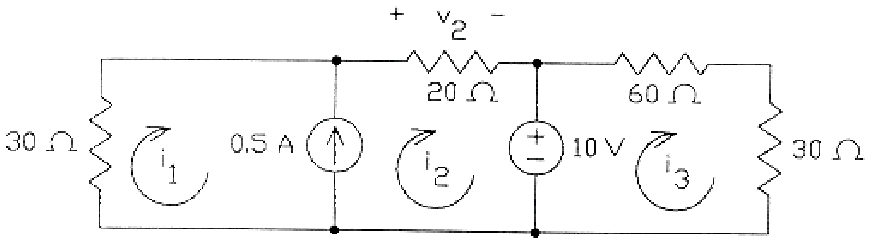

loop1 $\quad i_1 - i_2 = -0.5 \Rightarrow i_1 = i_2 - 0.5$

loop1,2 $\quad 30\,i_1 + 20\,i_2 + 10 = 0$

$30(i_2 - 0.5) + 20 i_2 = -10$

$50 i_2 - 15 = -10$

$i_2 = \frac{5}{50} = .1$ A

$i_1 = -.4$ A

$v_2 = 20 i_2 = \underline{2\text{ V}}$

P4.7-4 $\quad i_b = i_a - 0.02$

$250\,i_a + 100\,(i_a - 0.02) + 9 = 0$

$\therefore i_a = -.02\text{ A} = -20\text{ mA}$

$v_c = 100(i_a - 0.02) = \underline{-4\text{ V}}$

P4.7-5

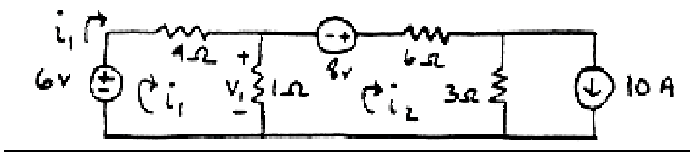

KVL mesh i_1 : $-6+4i_1+(i_1-i_2)=0 \Rightarrow \underline{-6+5i_1-i_2=0}$ (1)

KVL mesh i_2: $(i_2-i_1)-8+6i_2+3(i_2-10)=0 \Rightarrow \underline{-38-i_1+10i_2=0}$ (2)

Solving (1) & (2) simultaneously yields $\underline{i_1 = 2\text{ A}}$ and $i_2 = 4$ A $\therefore \underline{v_1 = 1(i_1-i_2) = -2\text{ V}}$

P4.7-6

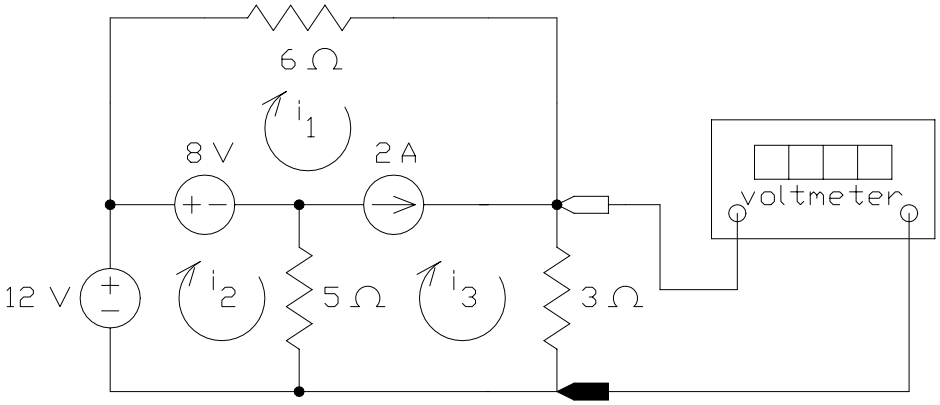

Express the current source current in terms of the mesh currents:

$$i_3 - i_1 = 2 \quad \Rightarrow \quad i_1 = i_3 - 2$$

Supermesh: $6i_1 + 3i_3 - 5(i_2 - i_3) - 8 = 0 \quad \Rightarrow \quad 6i_1 - 5i_2 + 8i_3 = 8$

Lower, left mesh: $-12 + 8 + 5(i_2 - i_3) = 0 \quad \Rightarrow \quad 5i_2 = 4 + 5i_3$

Eliminating i_1 and i_2 from the supermesh equation:

$$6(i_3 - 2) - (4 + 5i_3) + 8i_3 = 8 \quad \Rightarrow \quad 9i_3 = 24$$

The voltage measured by the meter is: $3i_3 = 3\dfrac{24}{9} = 8$ V

P4.7-7

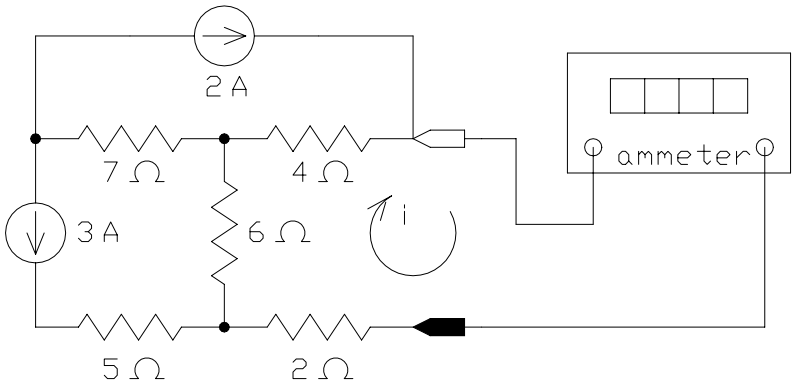

Mesh equation for right mesh:

$$4(i-2)+2i+6(i+3)=0 \;\Rightarrow\; 12i-8+18=0 \;\Rightarrow\; i=\frac{10}{12}\text{ A}$$

P4.7-8

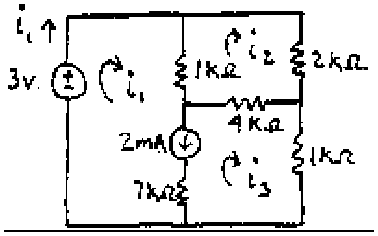

KVL around mesh i_1 & i_3 combined

$-3+(i_1-i_2)+4(i_3-i_2)+i_3=0$

yields $3-i_1+5i_2-5i_3=0$ (1)

KVL around mesh i_2

$i_2-i_1+2i_2+4(i_2-i_3)=0$

yields $i_1-7i_2+4i_3=0$ (2)

also $i_1-i_3=2$ (3)

Solving (1), (2), & (3) simultaneously yields $i_1 = 3$ mA

Section 4-7 Mesh Current Analysis with Voltage and Current Sources
b) Independent and Dependent Sources

P4.7-9

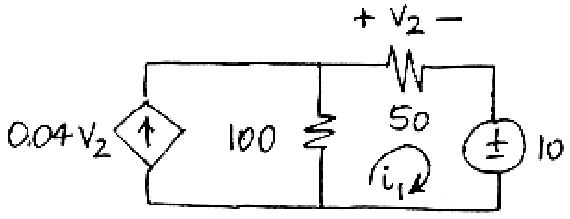

$v_2 = 50i_1$

$-100\,(0.04(50i_1)-i_1)+50i_1+10=0 \Rightarrow i_1 = 0.2$ A

$v_2 = 50\,i_1 = 10$ V

P4.7-10

$$i_b = 4i_b - i_a \Rightarrow i_b = \frac{1}{3}i_a$$

$$-100\left(\frac{1}{3}i_a\right)+200i_a+8=0 \Rightarrow i_a = -0.048\text{ A}$$

P4.7-11

$$i_b = .06 - i_a$$

$$-100\,(0.06 - i_a) + 50\,(0.06 - i_a) + 250\,i_a = 0$$

$$\therefore i_a = 10 \text{ mA}$$

$$v_o = 50 i_b = 50(.06 - .01) = \underline{2.5 \text{ V}}$$

P4.7-12

$$v_b = 100\,(.006 - i_a)$$

$$-100\,(.006 - i_a) + 3\left[100(.006 - i_a)\right] + 250 i_a = 0$$

$$\therefore \underline{i_a = -24 \text{ mA}}$$

P4.7-13

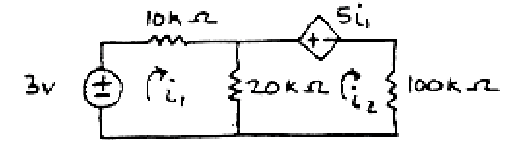

KVL i_1: $-3 + 10i_1 + 20(i_1 - i_2) = 0 \Rightarrow \underline{30i_1 - 20i_2 = 3}$ (1)

KVL i_2: $5i_1 + 100i_2 + 20(i_2 - i_1) = 0 \Rightarrow \underline{i_1 = 8i_2}$ (2)

Solving (1) & (2) simultaneously $\Rightarrow i_1 = \frac{6}{55}$ mA, $i_2 = \frac{3}{220}$ mA

$$\therefore P_{\text{deliv. to 5i and 100k}\Omega} = (5i_1)(i_2) + 100(i_2)^2$$

$$= 5\left(\tfrac{6}{55}\right)\left(\tfrac{3}{220}\right) + 100\left(\tfrac{3}{220}\right)^2 = 0.026 \text{ mA}$$

$$= 2.6\times10^{-5} \text{ W}$$

$$\therefore \text{Energy in 24 hr.} = Pt = \left(2.6\times10^{-5}\right)(24 \text{ hr})\left(3600 \text{ s}/\text{hr}\right)$$

$$= \underline{2.25 \text{ J}}$$

P4.7-14 (a)

$$v_o = -gR_L v \text{ and } v = \frac{R_2}{R_1 + R_2} v_i \Rightarrow \frac{v_o}{v_i} = -g\frac{R_L R_2}{R_1 + R_2}$$

(b)

$$\text{So have } \frac{v_o}{v_i} = -g\frac{\left(5\times10^3\right)\left(10^3\right)}{1.1\times10^3} = -170 \Rightarrow \underline{g = 0.0374 \text{ S}}$$

P4.7-15

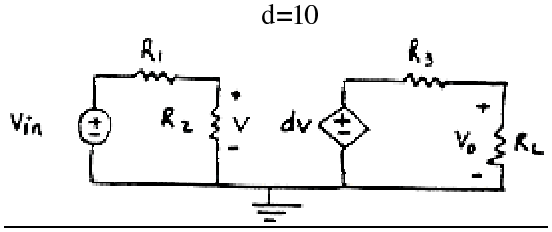

$$\text{from voltage divider } v = v_{in}\frac{R_2}{R_1 + R_2}$$

$$\text{from voltage divider } v_o = dv\frac{R_L}{R_L + R_3}$$

$$= (10)v_{in}\frac{R_2}{R_1 + R_2} \cdot \frac{R_L}{R_L + R_3}$$

$$\therefore \underline{\frac{v_o}{v_{in}} = \frac{10R_L R_2}{(R_L + R_3)(R_1 + R_2)}}$$

Section 4-8 Node Voltage Method and Mesh Current Method Compared

P4.8.1

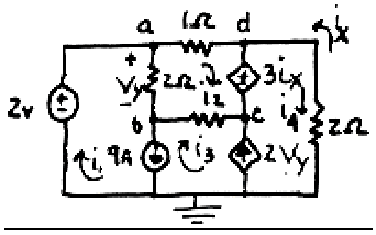

a) Mesh Analysis

Combine loop 1, 3, & 4 into supermesh

$$\Rightarrow -2+(i_1-i_2)2+(i_3-i_2)-3i_x+2i_4=0 \quad (1)$$

loop i_2: $-2i_1+4i_2-i_3+3i_x=0 \quad (2)$

also: $i_1-i_3=9 \quad (3)$

$$i_4-i_3=2v_y \quad (4)$$

$$2(i_1-i_2)=v_y \quad (5)$$

and $v_c=-2i_x-3i_x \quad (6)$

$i_4=-i_x \quad (7)$

Solving $(1)-(7)$ simultaneously yields

$i_x=-1$ A, $v_c=5$ V

b) Nodal Analysis

$v_a = 2$V

KCL at b: $9+\frac{v_b-v_c}{1}+\frac{v_b-2}{2}=0\Rightarrow 3v_b-2v_c=-16 \quad (1)$

form super node around nodes c & d, then KCL yields

$$\frac{v_d-2}{1}+\frac{v_d}{2}-2v_y+\frac{v_c-v_b}{1}=0$$

with $v_y=2-v_b$ and multiplying above through by 2 yields

$$2v_b+2v_c+3v_d=12 \quad (2)$$

also: $v_d-v_c=3i_x=3\left(-v_d/2\right)\Rightarrow v_c+2.5v_d=0 \quad (3)$

Solving $(1)-(3)$ yields

$v_c=5$ V and $v_d=2v\Rightarrow i_x=-\frac{v_d}{2}=-1$ A

PSpice Problems

SP 4-1 Spice deck corresponding to Problem SP 4-1

```
V1     1     0     dc    6
R2     1     2           3
I3     0     2     dc    1
V4     3     2     dc    3
R5     3     0           6
R6     3     1
.END
```

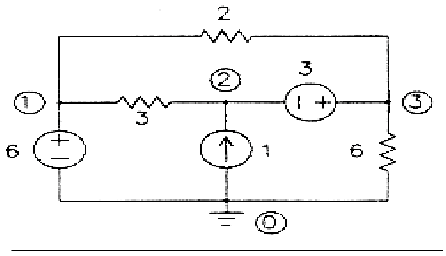


```
   NODE  VOLTAGE        NODE    VOLTAGE
(    1)   6.0000    (     2)     4.0000
(    3)   7.0000

    VOLTAGE SOURCE CURRENTS
    NAME           CURENT
    V1          -1.667E-01
    V4          -1.667E+00
```

SP 4-2 Spice Deck Corresponding to Problem SP 4-2

```
VI     1     0     dc  40
R2     1     2         220
R3     2     0         150
R4     2     3         330
R5     3     0          75
R6     1     3         100
.END
```

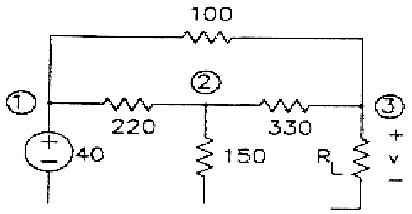


```
   NODE  VOLTAGE      NODE    VOLTAGE      NODE    VOLTAGE
(    1)  40.0000   (    2)    16.3950    (   3)    17.0570

   VOLTAGE SOURCE CURRENTS
   NAME           CURRENT
   V1          -3.367E-01
```

SP 4-3 Spice Deck corresponding to Problem SP 4-3

```
V1    1   0   dc     5
R3    2   0         2K
R4    2   3         6K
R5    3   0         3K
.END
```

V=0.588V

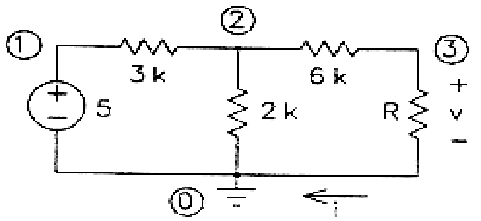

SP 4-4 Spice deck corresponding to Problem SP 4-4

```
R1  1  0  2
R2  1  2  3
R3  1  5  1
R4  2  0  3
R5  2  3  2
R6  2  5  1
V7  4  3  4
R8  4  0  1
V9  4  6  4
R10 5  6  2
. END
```

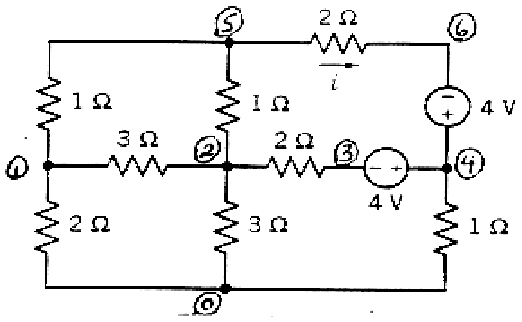

```
  NODE    VOLTAGE        NODE    VOLATAGE       NODE    VOLTAGE
(    1)  -1.2332       (    2)  -1.6364       (    3)  -2.8379
(    4)   1.1621       (    5)  -1.7154       (    6)  -2.8379

 VOLTAGE SOURCE CURRENTS
 NAME         CURRENT
 V7          -6.008E-O.1
 V9          -5.613E-0.1
```

SP 4-5

Input File:

```
R1        0     5          6000
R2        1     6          3000
R3        1     2          2000
R4        3     4          2000
R5        4     5          8000
V1        2     3     dc   16
V2        6     4     dc   8
I1        5     4     dc   1m
Vsc1      1     0          0
H1        3     6     Vsc1 4

.dc V1 16 16 1
.print dc I(Vsc1)
.end
```

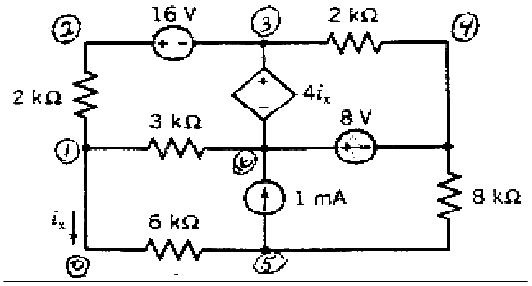

Output:

```
  V1         I(Vsc1)
  1.600E+1   1.684E-03
```

SP 4-6

Input File:

```
R1        0      1              1
R2        3      4              7
R3        4     10              5
R4       10      7              3
R5        6      7              4
R6       10      9              2
R7        7      8              6
V1        9     11      dc      6
V2        2      1      dc     10
Vsc1      2      3              0
Vsc2     11      0              0
Vsc3      5      6              0
H1        1     10      Vsc2   4
F1        8      9      Vsc1   2
E1        4      5     7    8   3
.dc V1 6 6 1
.print dc I Vsc2
.end
```

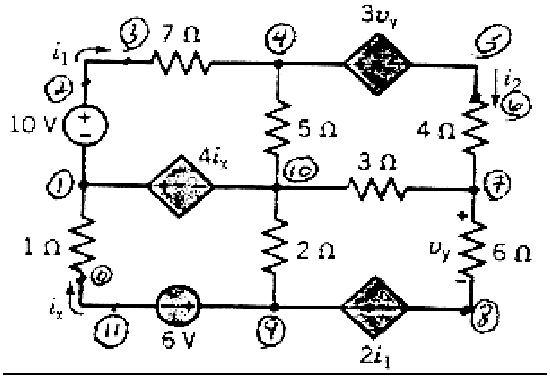

Output:

```
   V1          I(Vsc2)
   6.000+E00 -6.706E-01
```

SP 4-7 Spice deck corresponding to Problem SP 4-7

```
R1      1 0 2
R2      4 2 1
VSC3    1 4 0
F3      2 0 VSC3   4
R4      2 3 2
R5      3 0 2
I6      3 1 DC     3
.END
```

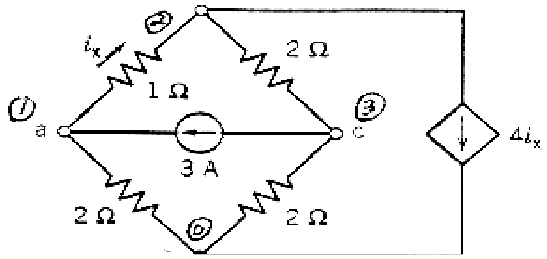


```
 NODE    VOLTAGE       NODE       VOLTAGE       NODE       VOLTAGE
(    1)     8.6667    (    2)       10.0000    (    3)         2.0000
(    4)     8.6667

 VOLTAGE SOURCE CURRENTS
 NAME          CURRENT

 VSC3         -1.333E+00
```

Verification Problems

VP 4-1

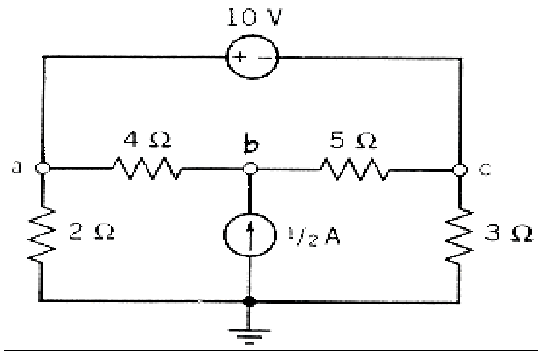

Apply KCL at node b

$$\frac{v_b - v_a}{4} - \frac{1}{2} + \frac{v_b - v_c}{5} = 0$$

$$-\frac{4.8-5.2}{4} - \frac{1}{2} + \frac{-4.8-3.0}{5} \neq 0$$

The given voltages do not satisfy the KCL equation at node b. They are not correct.

VP 4-2

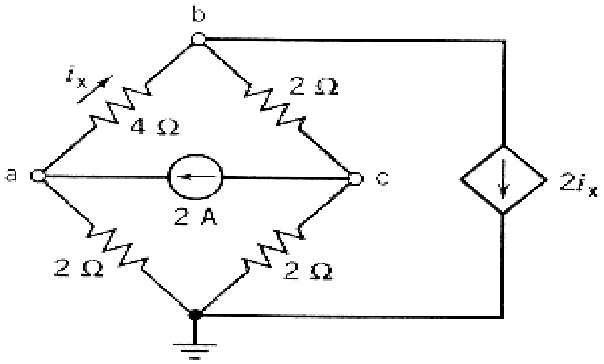

Apply KCL at node a:

$$-\left(\frac{v_b + v_a}{4}\right) - 2 + \frac{v_a}{2} = 0$$

$$-\left(\frac{20-4}{4}\right) - 2 + \frac{4}{2} = -4 \neq 0$$

The given voltages do not satisfy the KCL equation at node a. They are not correct.

VP 4-3

Writing a node equation:

$$-\left(\frac{12-7.5}{R_1}\right) + \frac{7.5}{R_3} + \frac{7.5-6}{R_2} = 0$$

so

$$-\frac{4.5}{R_1} + \frac{7.5}{R_3} + \frac{1.5}{R_2} = 0$$

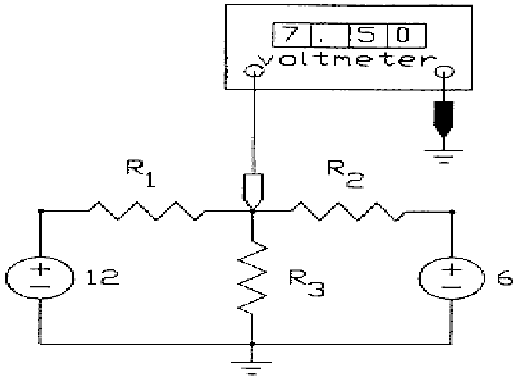

There are only three cases to consider. Suppose $R_1 = 5\text{k}\Omega$ and $R_2 = 10\text{k}\Omega$. Then

$$-\frac{4.5}{R_1} + \frac{7.5}{R_3} + \frac{1.5}{R_2} = -0.9 + 0.75 + 0.15 = 0$$

This choice of resistance values corresponds to branch currents that satisfy KCL. Therefore, it is indeed possible that two of the resistance are 10kΩ and the other resistance is 5kΩ. The 5kΩ is R .

VP 4-4

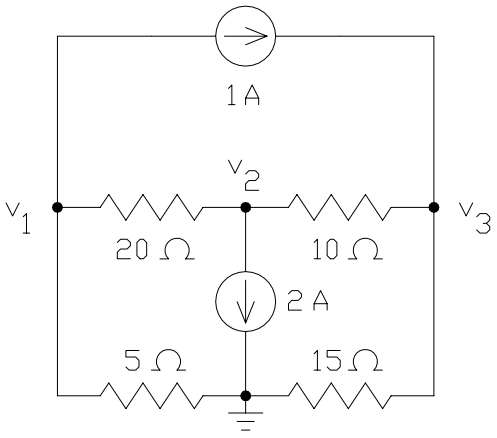

KCL at node 1:

$$0=\frac{v_1-v_2}{20}+\frac{v_1}{5}+1=\frac{-8-(-20)}{20}+\frac{-8}{5}+1$$

KCL at node 2:

$$\frac{-8-(-20)}{20}=2+\frac{-20-(-6)}{10}\quad\Rightarrow\quad\frac{12}{20}=\frac{6}{10}$$

KCL at node 3: $\dfrac{-20-(-6)}{10}+1=\dfrac{-6}{15}\quad\Rightarrow\quad\dfrac{-4}{10}=\dfrac{-6}{15}$

KCL is satisfied at all of the nodes so the computer analysis is correct.

VP 4-5

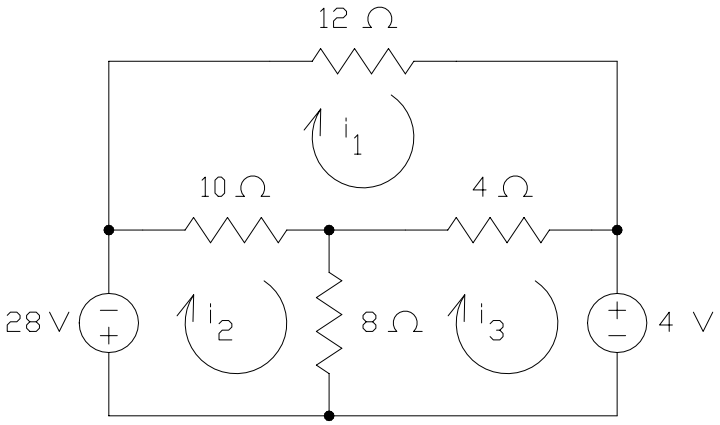

Top mesh: $10(2-4)+12(2)+4(2-3)=0$

Bottom right mesh $8(3-4)+4(3-2)+4=0$

Bottom, left mesh: $28+10(4-2)+8(4-3)\neq 0$ (Perhaps the polarity of the 28 V source was entered incorrectly.)

KVL is not satified for the bottom, left mesh so the computer analysis is not correct.

Design Problems

DP 4-1

Simplify to

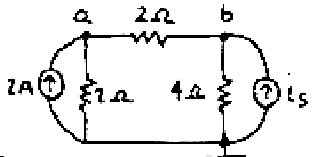

KCL at node a : $v_a\left(\frac{1}{2}+\frac{1}{2}\right)-\frac{1}{2}v_b-2=0$ (1)

at node b: $-\frac{1}{2}v_a+\left(\frac{1}{2}+\frac{1}{4}\right)v_b-i_s=0$ (2)

now $v_{ba}=3=v_b-v_a \Rightarrow v_b=3+v_a$ (3)

Plugging (3) into (1) yields: v_a=7 V & v_b=10 V

thus from (2) get: i_s=4 A

DP 4-2

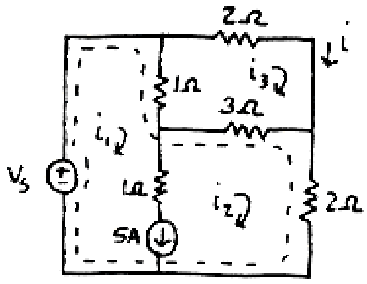

$i_3=i$ = 3A

Supermesh: $-v_s+1(i_1-i_3)+3(i_2-i_3)+2i_2=0$

$-v_3+i_1+5i_2=12$ (1)

mesh 3:1 $(i_3-i_1)+2i_3+3(i_3-i_2)=0$

$i_1+3i_2=18$ (2)

also $i_1-i_2=5$ (3)

Combining (2) & (3) yields i_2=3.25 A, i_1=8.25 A

from (1) v_s=12.5 V

DP 4-3

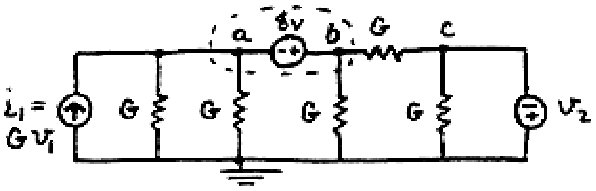

G = .5 S

$i_1 = Gv_1$

$v_c=-v_2$

Supernode : $v_a(G+G)+v_b(G+G)-Gv_c=i_1$ (1)

also : v_b-v_a=8 (2)

Combining (1) & (2) yields $v_a+(8+v_a)+.5v_2=.5v_1$

$2v_a=.5v_1-.5v_2-8$

$\Rightarrow v_a=\frac{.5v_1-.5v_2-8}{2}=0$

$\therefore .5v_1-.5v_2=8$

so let v_2 = 2 V and v_1 = 18 V (one solution)

DP 4-4

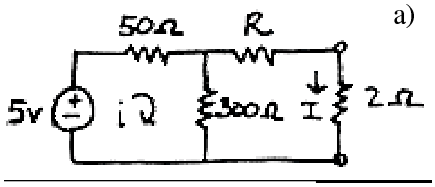

a) KVL left mesh : $-5+50i + 300\,(i-I) = 0$ (1)

right mesh : $(R+2)\,I + 300\,(I-i) = 0$ (2)

Solving (1) & (2) for I $\Rightarrow$ $I = \dfrac{150}{1570 + 35\,R}$ (3)

Desire $50\text{mA} \le I \le 75\text{mA}$

so if R = 100, then I = 29.59 mA $\Rightarrow$ lamp will not light

b) from (3) note that as R↓ I↑, so try $R = 50\ \Omega \Rightarrow I = 45$ mA (won't light)

try $R = 25\Omega \Rightarrow I = 61$ mA $\Rightarrow$ will light

Now check if R±10% will light and not burn out

$-10\% \rightarrow 22.5\Omega \rightarrow I = 63.63$ mA } lamp will

$+10\% \rightarrow 27.5\Omega \rightarrow I = 59.23$ mA } stay on

DP 4-5

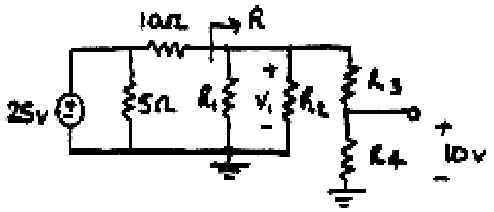

$R = R_1 // R_2 // (R_3 + R_4)$

$$v_1 = 25\frac{R}{10+R}$$

Using voltage divider

$$10 = \frac{R_4}{R_3+R_4}\,v_1 = \frac{R_4}{R_3+R_4}\,\frac{\left(R_1 \| R_2 \| (R_3+R_4)\right)}{10 + \left(R_1 \| R_2 \| (R_3+R_4)\right)}\,25$$

one solution: choose $R_1 = R_2 = 25\Omega \rightarrow 10 = \dfrac{R_4}{20}\,\dfrac{(12.5 \| 20)}{10 + (12.5 \| 20)}\,25 \Rightarrow R_4 = 18.4\Omega$

$\& \; R_3 + R_4 = 20 \Rightarrow R_3 = 1.6\Omega$

DP 4-6

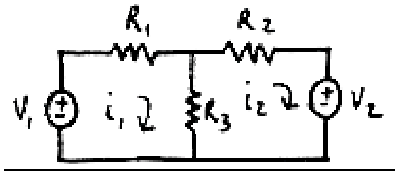

mesh i_1: $(R_1+R_3)\,i_1 - R_3 i_2 - v_1 = 0$ (1)

mesh i_2: $-R_3 i_1 + (R_2+R_3)\,i_2 + v_2 = 0$ (2)

from (1) & (2) get : $i_1 = \dfrac{\begin{bmatrix} v_1 & -R_3 \\ -v_2 & (R_2+R_3) \end{bmatrix}}{\Delta}$ $\qquad i_2 = \dfrac{\begin{bmatrix} (R_1+R_3) & v_1 \\ -R_3 & -v_2 \end{bmatrix}}{\Delta}$

where $\Delta = (R_1+R_3)(R_2+R_3) - R_3^2$

Now if $R_1 = R_2 = R_3 = 1K$ where K represents 1000

then $\Delta = 4-1 = 3K^2$

so we have $i_1 = \dfrac{[2v_1 - v_2]\,K}{3K^2}$, $i_2 = \dfrac{[-2v_2 + v_1]\,K}{3K^2}$

$\Rightarrow i = i_1 - i_2 = \dfrac{v_1+v_2}{3K}$

if $v_1 = v_2 = 1$ V $\Rightarrow i = \frac{2}{3}$ mA okay

if $v_1 = v_2 = 2$ V $\Rightarrow i = \frac{4}{3}$ mA okay

DP 4-7

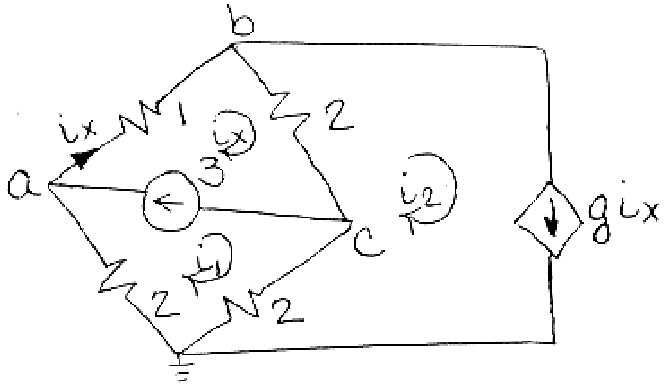

$v_a - v_c = \dfrac{20}{3}$

$i_x - i_1 = 3$ $\qquad v_a = -2i_1$

$i_2 = g i_x$ $\qquad v_c = 2i_1 - 2i_2$

$i_x + 2i_x - 2i_2 + 2i_1 - 2i_2 + 2i_1 = 0$

Substituting solve for g : g=4